



PENNSYLVANIA SCIENCE OLYMPIAD 2006 STATE FINALS
CIRCUIT LAB C DIVISION

ANSWER SHEET

SECTION 1

SECTION 2

1. SCHEMATIC DIAGRAM

/5



/2 6.

/2 7.

/2 8.

/2 9.

/2 10.

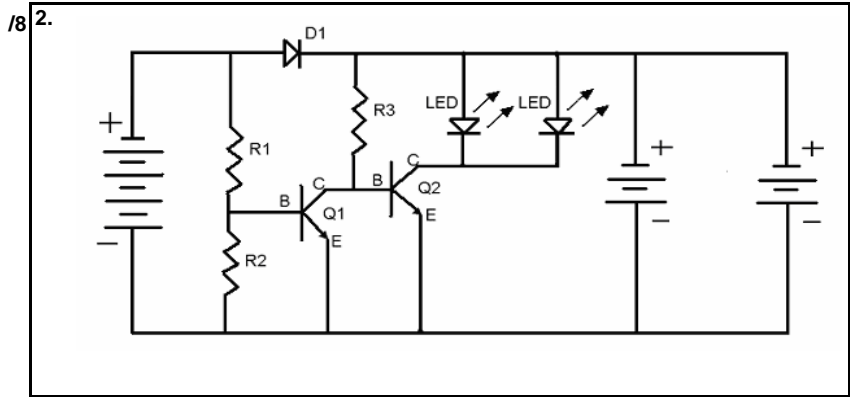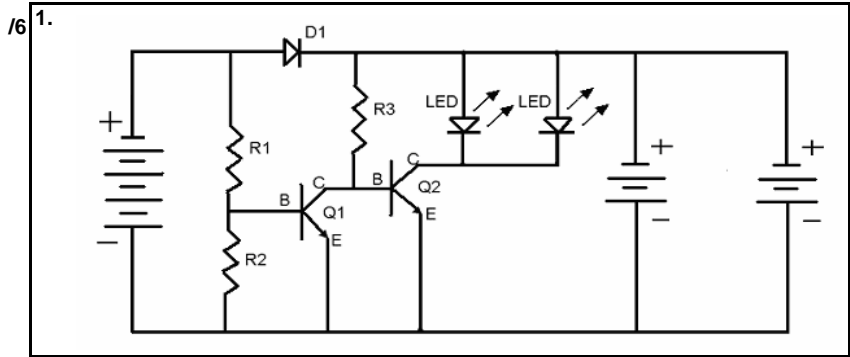

2. THEORETICAL QUANTITIES

/18

Resistor	Resistance Ω	Current A	Voltage V
R ₁			
R ₂			
R ₃			
R ₄			
R ₅			
R ₆			

SCHOOL CODE

SCHOOL NAME

PARTICIPANTS

/3 3.

/3 4.

/3 5.

/2 3.

/4 4.

/2 5.



**PENNSYLVANIA SCIENCE OLYMPIAD 2006 STATE FINALS
CIRCUIT LAB C DIVISION**

ANSWER SHEET

SECTION 3

/2 1.

/2 2.

/4 3.

/2 4.

/2 5.

/2 6.

/2 7.

/2 8.

/2 9.

/4 10.

+5 BONUS

SECTION 4

/2 1.

/2 2.

/2 3.

/2 4.

/2 5.

/2 6.

/2 7.

/2 8.

/2 9.

/2 10.

/2 11.

/2 12.

/2 13.

/18 14. - 19. THEORETICAL QUANTITIES

Resistor	Current	Voltage Drop
R ₁	<input style="width: 90%; height: 20px;" type="text"/>	<input style="width: 90%; height: 20px;" type="text"/>
R ₂	<input style="width: 90%; height: 20px;" type="text"/>	<input style="width: 90%; height: 20px;" type="text"/>
R ₃	<input style="width: 90%; height: 20px;" type="text"/>	<input style="width: 90%; height: 20px;" type="text"/>

/4 20.

/8 21. - 24. Voltmeter Resistances

Resistor	Resistance
R ₁	<input style="width: 90%; height: 20px;" type="text"/>
R ₂	<input style="width: 90%; height: 20px;" type="text"/>
R ₃	<input style="width: 90%; height: 20px;" type="text"/>
R ₄	<input style="width: 90%; height: 20px;" type="text"/>

/2 25.

/2 26.

/3 27.

/2 28.

/2 29.

/2 30.